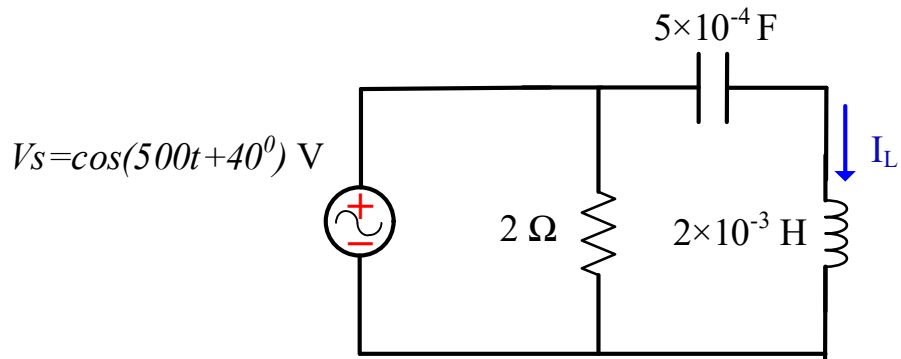



Q6 (20 marks) See the circuit below

1) Finding I_L in waveform. (14 marks)



2) What is the time period (T) of I_L ? What is the value of I_L when $t = 0 \text{ s}$? (6 marks)

Q7 (30 marks?) See the circuit below:

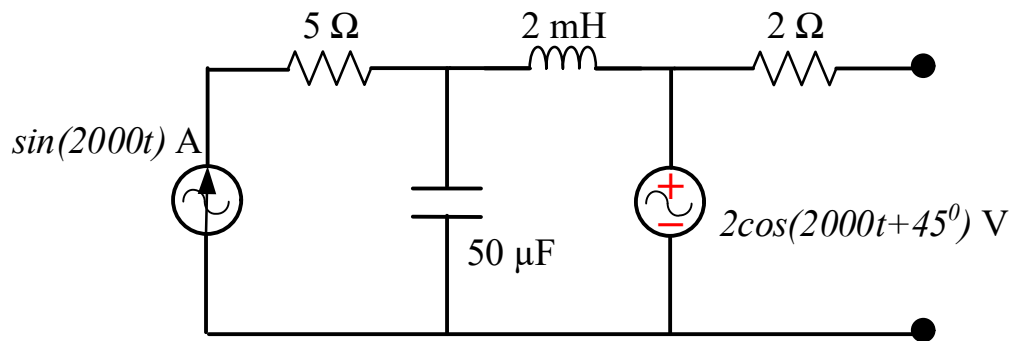

- 1) Finding the Thevenin voltage (7 marks), Norton current (7 marks) and Thevenin impedance (7 marks) of this circuit.
- 2) Draw the Thevenin's and Norton's equivalent circuit. (4 marks)
- 3) If we put a load impedance Z_L (it can be a complex value) between the two terminals, what is the value of the load to ensure maximum power to be delivered to the load. (5 marks)