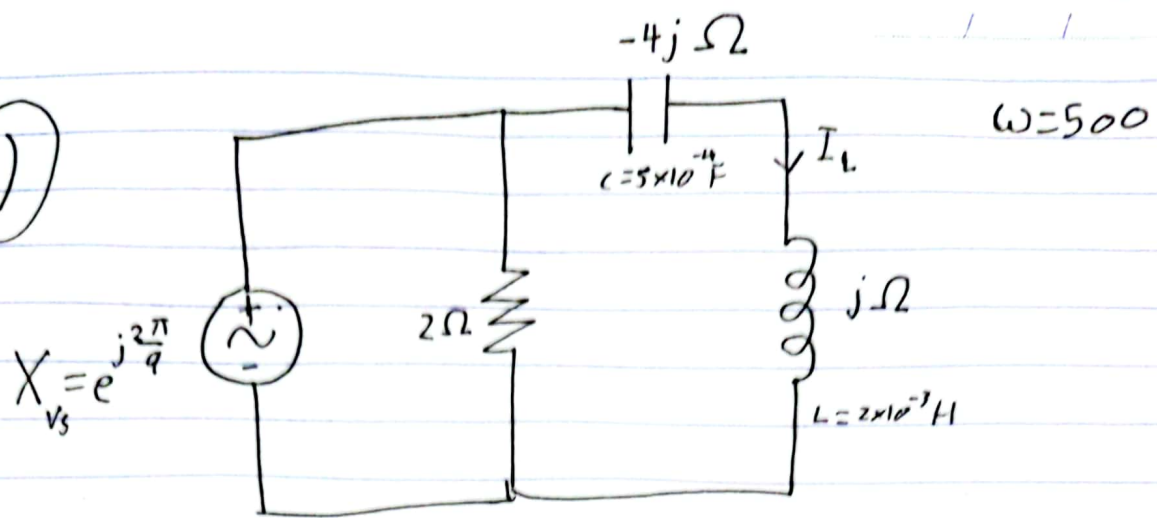


(6)




$$1) V_L = e^{j\frac{2\pi}{9}} \frac{j}{-3j} = -e^{j\frac{2\pi}{9}}$$

$$\therefore I_L = \frac{-e^{j\frac{2\pi}{9}}}{j} = \frac{-e^{j\frac{2\pi}{9}}}{3e^{j\frac{\pi}{2}}} = -\frac{e^{-j\frac{5\pi}{18}}}{3} = -\frac{e^{j\frac{31\pi}{18}}}{3} \quad (\text{current divider})$$

$$\therefore I_L = \frac{1}{3} \cos(500t + 310^\circ) \text{ A}$$

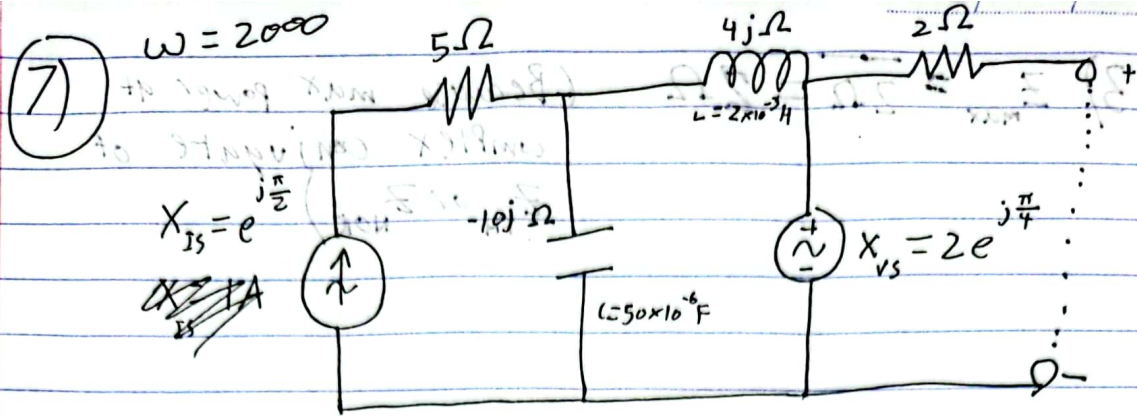
$$2) t=0 \Rightarrow I_L = \frac{\cos(310^\circ)}{3} \approx \frac{-0.2142625}{3} \approx -0.0714208$$



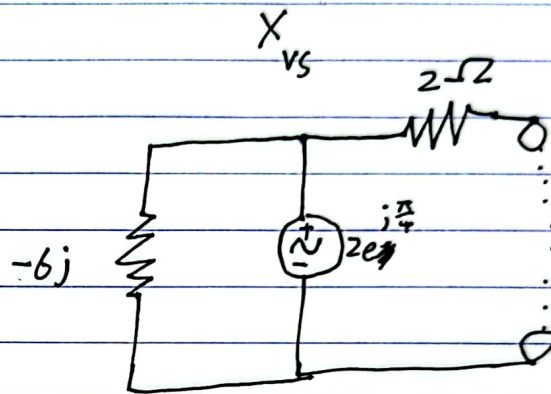1) $Z_{TH} = Z_{NOR} = \cancel{5} \parallel \cancel{-10j} + 4j = 2 \Omega$ (since all current flows through no-resistance zeroed wire)

Superposition

With X_{IS} , no current reaches terminals.




$\therefore I_{NOR} = e^{j\pi/4}$ (because $\frac{2e^{j\pi/4}}{2} = \frac{V}{Z} = e^{j\pi/4}$)

$I_{NOR} = \cos(2000t + 45^\circ) A$


$\therefore V_{TH} = 2 \cos(2000t + 45^\circ) V$

2)


Norton

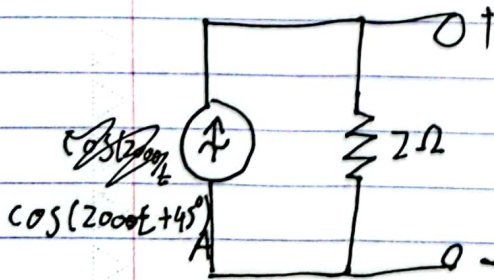

Thévenin

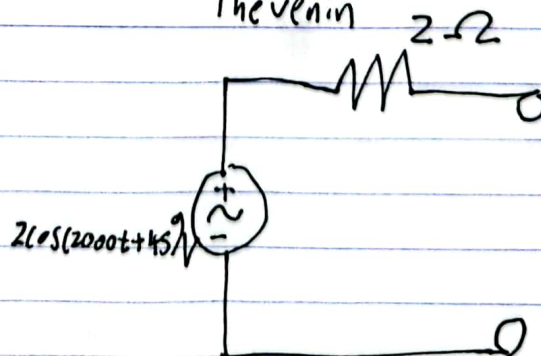
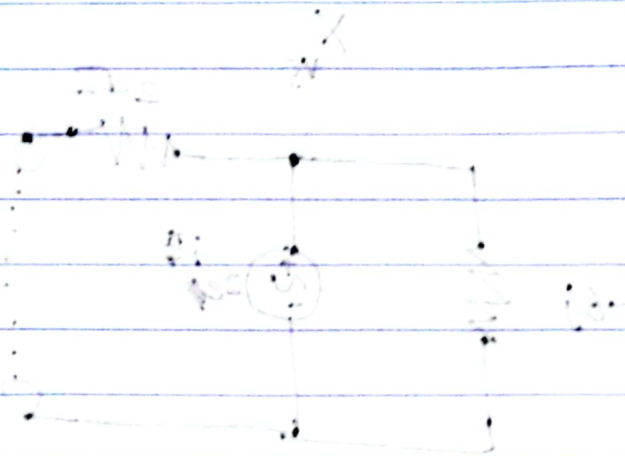
$$3) Z_{\max} = \overline{Z_{\text{TH}}} = 2\Omega \quad (\text{Because max power at complex conjugate of } Z_{\text{TH}} \text{ or } Z_{\text{NOR}})$$



$$V_{\text{TH}} = 10V$$