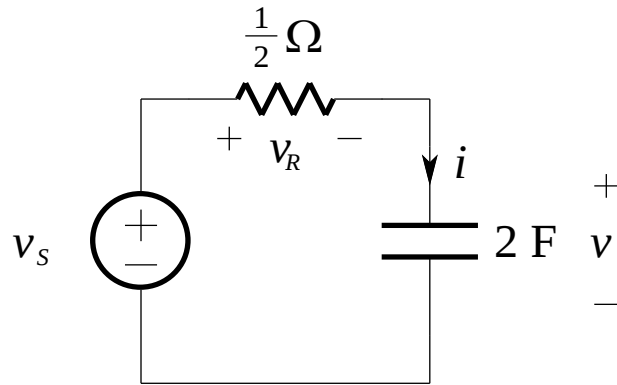


Capacitance


Worked Solutions

1.

Consider the circuit shown below:




Suppose that the voltage $v(t)$ is:

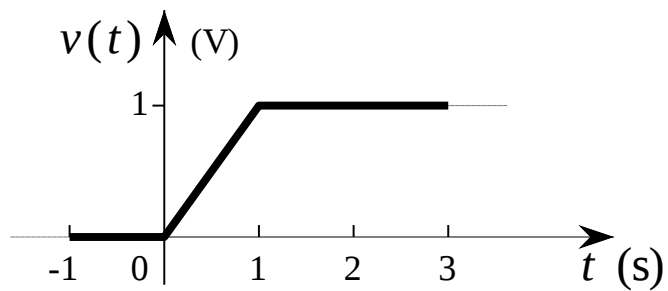


Find $i(t)$, $w_C(t)$, $p_R(t)$, $v_R(t)$ and $v_S(t)$, and sketch these functions.

1.

Consider the circuit shown below:

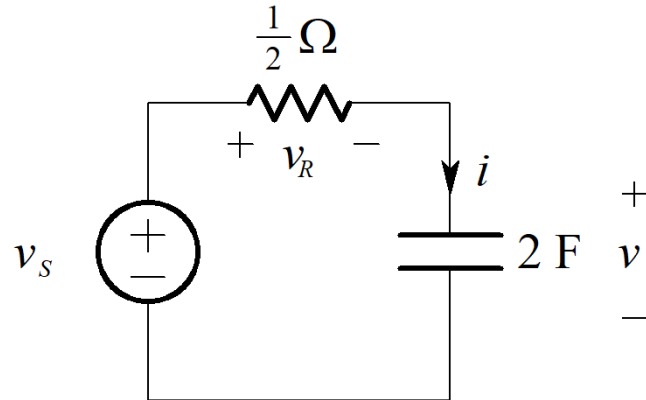

Suppose that the voltage $v(t)$ is:

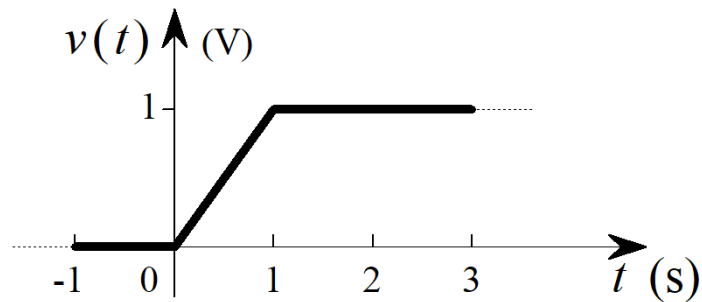

Find $i(t)$, $w_C(t)$, $p_R(t)$, $v_R(t)$ and $v_s(t)$, and sketch these functions.

Solution

The function $v(t)$ can be separated into three parts: the constant voltage from $t = -1$ to $t = 0$, the linear function from $t = 0$ to $t = 1$, and the constant voltage from $t = 1$ to $t = 3$. For the linear function, it is increasing at a rate of 1 V s^{-1} , which is equivalent to $v(t) = 1t$. Re-writing this information into a function:

$$v(t) = \begin{cases} 0 \text{ V} & \text{for } -1 < t < 0 \\ t \text{ V} & \text{for } 0 < t < 1 \\ 1 \text{ V} & \text{for } 1 < t < 3 \end{cases}$$

(a) $i(t)$

The formula for current through a capacitor is:

$$i(t) = C \frac{dv}{dt}$$

for $-1 < t < 0$,

$v(t)$ is constant at 0 V, there is no rate of change therefore $\frac{dv}{dt} = 0$.

$$i(-1 < t < 0) = C \frac{dv}{dt}$$

$$i(-1 < t < 0) = 2 \times 0$$

$$i(-1 < t < 0) = 0 \text{ A}$$

for $0 < t < 1$,

$v(t)$ is linearly increasing at a rate of 1 Vs^{-1} , or $\frac{dv}{dt}(1t) = 1$.

$$i(0 < t < 1) = C \frac{dv}{dt}$$

$$i(0 < t < 1) = 2 \times 1$$

$$i(0 < t < 1) = 2 \text{ A}$$

for $1 < t < 3$,

$v(t)$ is constant at 1 V, there is no rate of change therefore $\frac{dv}{dt} = 0$.


$$i(1 < t < 3) = C \frac{dv}{dt}$$

$$i(1 < t < 3) = 2 \times 0$$

$$i(1 < t < 3) = 0 \text{ A}$$

$$i(t) = \begin{cases} 0 \text{ A} & \text{for } -1 < t < 0 \\ 2 \text{ A} & \text{for } 0 < t < 1 \\ 0 \text{ A} & \text{for } 1 < t < 3 \end{cases}$$

Therefore, graphing the function $i(t)$,

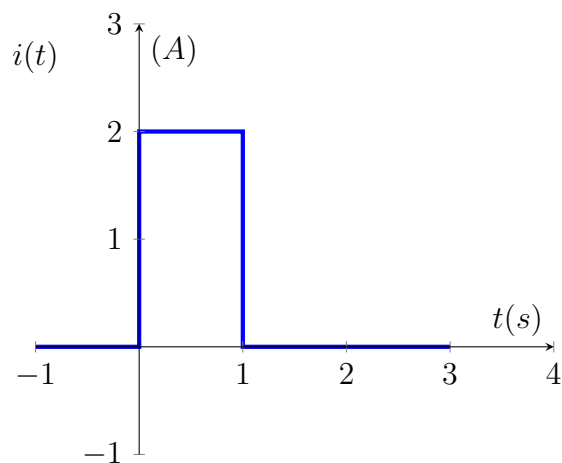

(b) $w_c(t)$

The formula for energy stored in a capacitor, w_c is:

$$w_c = \frac{1}{2} C v^2$$

for $-1 < t < 0$,

$$w_c(-1 < t < 0) = \frac{1}{2}(2)(0^2)$$

$$w_c(-1 < t < 0) = 0 \text{ J}$$

for $0 < t < 1$,

$$w_c(0 < t < 1) = \frac{1}{2}(2)(t^2)$$

$$w_c(0 < t < 1) = 1 \times t^2$$

$$w_c(0 < t < 1) = t^2 \text{ J}$$


for $1 < t < 3$,

$$w_c(1 < t < 3) = \frac{1}{2}(2)(1^2)$$

$$w_c(1 < t < 3) = 1 \text{ J}$$

$$w_c(t) = \begin{cases} 0 \text{ J} & \text{for } -1 < t < 0 \\ t^2 \text{ J} & \text{for } 0 < t < 1 \\ 1 \text{ J} & \text{for } 1 < t < 3 \end{cases}$$

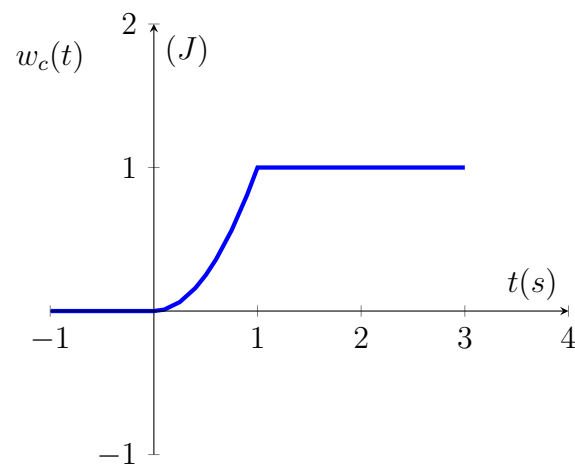Therefore, graphing the function $w_c(t)$,



(c) $p_R(t)$

To find the power emitted from the resistor, we can use the formula:

$$p = Ri^2$$

as the capacitor and resistor are in series, therefore $i_c(t) = i_R(t)$.

for $-1 < t < 0$,

$$p_R(-1 < t < 0) = R \times i(-1 < t < 0)^2$$

$$p_R(-1 < t < 0) = 0.5 \times 0$$

$$p_R(-1 < t < 0) = 0 \text{ W}$$

for $0 < t < 1$,

$$p_R(0 < t < 1) = R \times i(0 < t < 1)^2$$

$$p_R(0 < t < 1) = 0.5 \times 2^2$$

$$p_R(0 < t < 1) = 2 \text{ W}$$

for $1 < t < 3$,


$$p_R(1 < t < 3) = R \times i(1 < t < 3)^2$$

$$p_R(1 < t < 3) = 0.5 \times 0$$

$$p_R(1 < t < 3) = 0 \text{ W}$$

$$p_R(t) = \begin{cases} 0 \text{ W} & \text{for } -1 < t < 0 \\ 2 \text{ W} & \text{for } 0 < t < 1 \\ 0 \text{ W} & \text{for } 1 < t < 3 \end{cases}$$

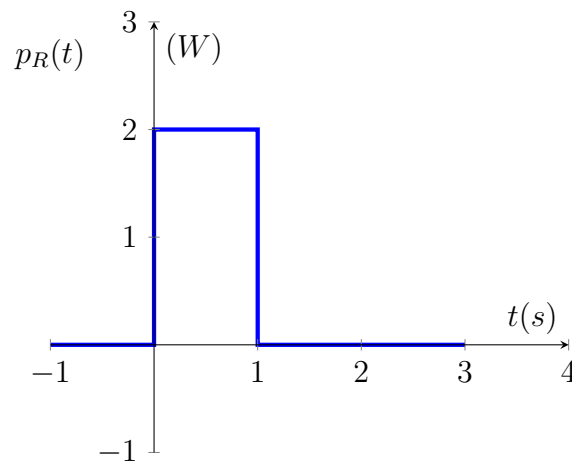Therefore, graphing the function $p_R(t)$



(d) $v_R(t)$

To find the voltage across the resistor, we can use Ohm's Law to solve for v .

$$\boxed{v = Ri}$$

for $-1 < t < 0$,

$$v_R(-1 < t < 0) = 0.5 \times i(-1 < t < 0)$$

$$v_R(-1 < t < 0) = 0.5 \times 0$$

$$v_R(-1 < t < 0) = 0 \text{ V}$$

for $0 < t < 1$,

$$v_R(0 < t < 1) = 0.5 \times i(0 < t < 1)$$

$$v_R(0 < t < 1) = 0.5 \times 2$$

$$v_R(0 < t < 1) = 1 \text{ V}$$

for $1 < t < 3$,


$$v_R(1 < t < 3) = 0.5 \times i(1 < t < 3)$$

$$v_R(1 < t < 3) = 0.5 \times 0$$

$$v_R(1 < t < 3) = 0 \text{ V}$$

$$\boxed{v_R(t) = \begin{cases} 0 \text{ V} & \text{for } -1 < t < 0 \\ 1 \text{ V} & \text{for } 0 < t < 1 \\ 0 \text{ V} & \text{for } 1 < t < 3 \end{cases}}$$

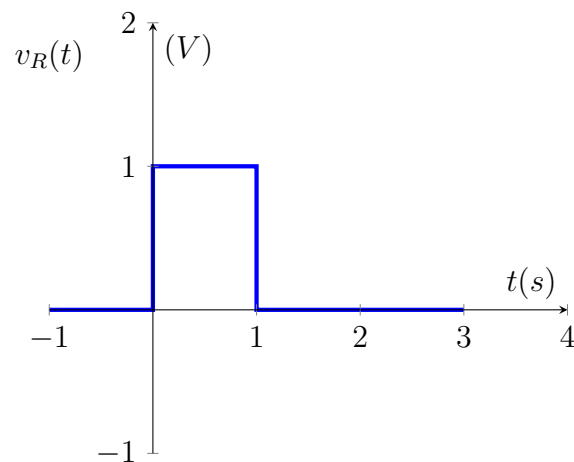Therefore, graphing the function $v_R(t)$



(e) $v_s(t)$

To solve for the voltage source, we can use KVL because we now know $v_c(t)$ and $v_R(t)$. Therefore:

$$\boxed{v_s(t) = v_c(t) + v_R(t)}$$

for $-1 < t < 0$,

$$v_s(-1 < t < 0) = v_c(-1 < t < 0) + v_R(-1 < t < 0)$$

$$v_s(-1 < t < 0) = 0 + 0$$

$$v_s(-1 < t < 0) = 0 \text{ V}$$

for $0 < t < 1$,

$$v_s(0 < t < 1) = v_c(0 < t < 1) + v_R(0 < t < 1)$$

$$v_s(0 < t < 1) = t + 1$$

$$v_s(0 < t < 1) = (t + 1) \text{ V}$$

for $1 < t < 3$,


$$v_s(1 < t < 3) = v_c(1 < t < 3) + v_R(1 < t < 3)$$

$$v_s(1 < t < 3) = 1 + 0$$

$$v_s(1 < t < 3) = 1 \text{ V}$$

$$\boxed{v_s(t) = \begin{cases} 0 \text{ V} & \text{for } -1 < t < 0 \\ t + 1 \text{ V} & \text{for } 0 < t < 1 \\ 1 \text{ V} & \text{for } 1 < t < 3 \end{cases}}$$

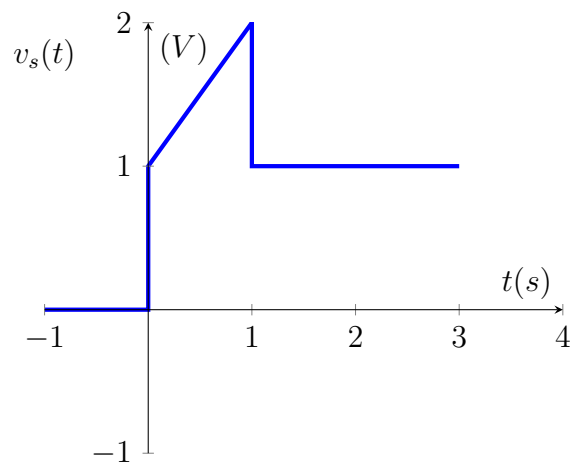Therefore, graphing the function $v_s(t)$



2.

The voltage $v(t)$ across a 2-F capacitor at time $t=1\text{ s}$ is $\frac{1}{4}\text{ V}$. If the current through the capacitor is:

$$i(t) = \begin{cases} t & \text{for } 1 \leq t < 2 \\ 0 & \text{for } 2 \leq t < \infty \end{cases}$$

find $v(t)$ for $t \geq 1\text{ s}$.


Capacitance

The voltage $v(t)$ across a 2 F capacitor at time $t = 1$ s is $\frac{1}{4}$ V. If the current through the capacitor is:

$$i(t) = \begin{cases} t & 1 \leq t < 2 \\ 0 & 2 \leq t < \infty \end{cases}$$

Find $v(t)$ for $t \geq 1$ s.

Solution

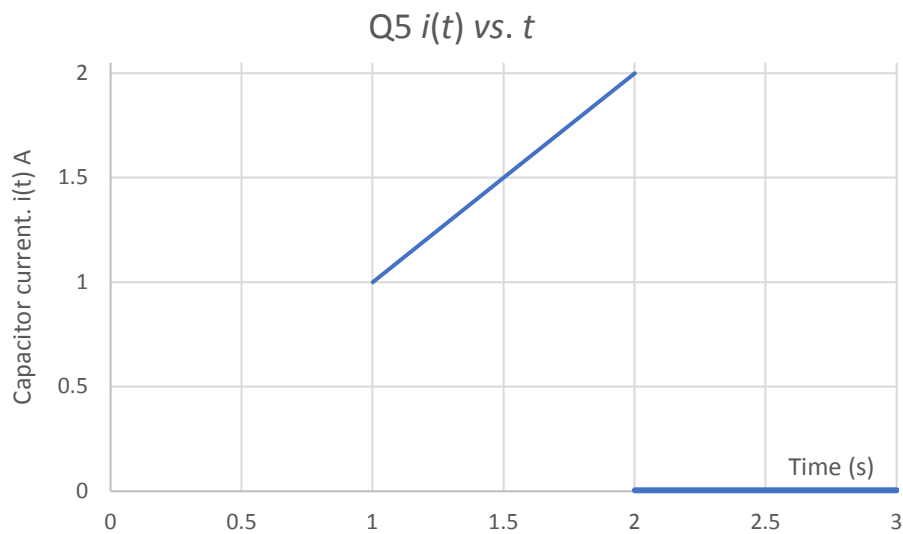

The equation we need for this is:

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0) \quad (1)$$

The first step is to find $v(t)$ for $1 \leq t < 2$:

The time origin for the equation is at $t = 1$ so $v(t_0) = v(1\text{s}) = \frac{1}{4}$ V, using equation 1

$$1 \leq t < 2 \quad i(t) = t \quad \Rightarrow 1 \leq t < 2 \quad i(\tau) = \tau$$

$$v(t) = \frac{1}{2} \int_1^t \tau d\tau + \frac{1}{4}$$

$$v(t) = \frac{1}{2} \left[\frac{\tau^2}{2} \right]_1^t + \frac{1}{4}$$

$$v(t) = \frac{1}{2} \left[\frac{t^2 - 1}{2} \right] + \frac{1}{4}$$

$$v(t) = \frac{t^2 - 1}{4} + \frac{1}{4}$$

$$v(t) = \frac{t^2}{4}$$

Thus, for

$$1 \leq t < 2 \quad v(t) = \frac{t^2}{4}$$


and

$$v(2) = 1 \text{ V}$$

For $t \geq 2$, $i(t) = 0$, thus no charge enters – or leaves - the capacitor and hence the voltage remains constant at 1 V.



$$v(t) = \begin{cases} \frac{t^2}{4} & 1 \leq t < 2 \\ 1 & 2 \leq t < \infty \end{cases}$$

Q5 $v(t)$ vs. t

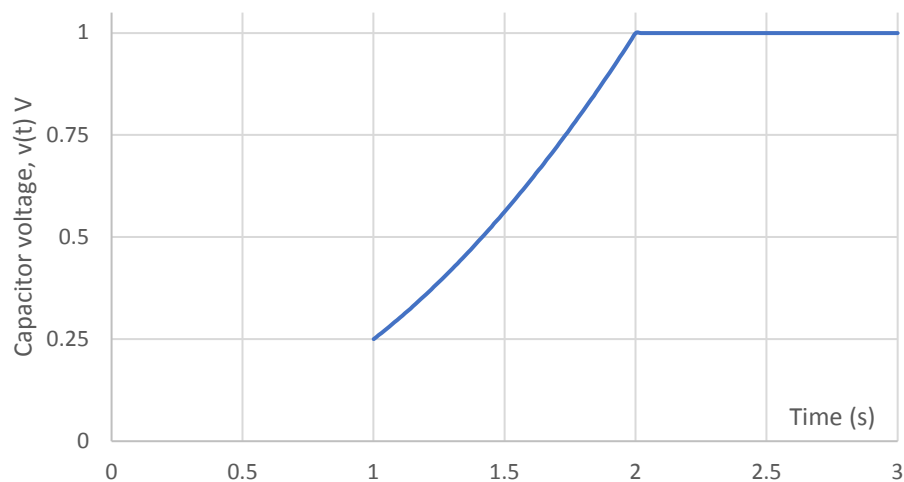


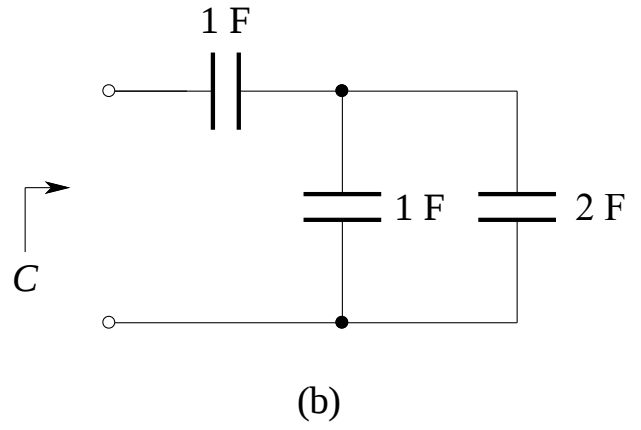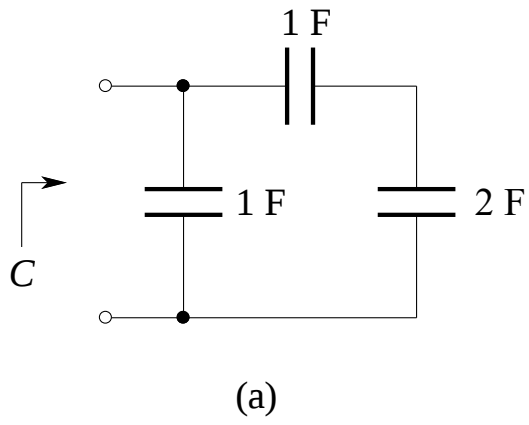3.


For each of the circuits shown below, what is the value of C ?



Solutions :

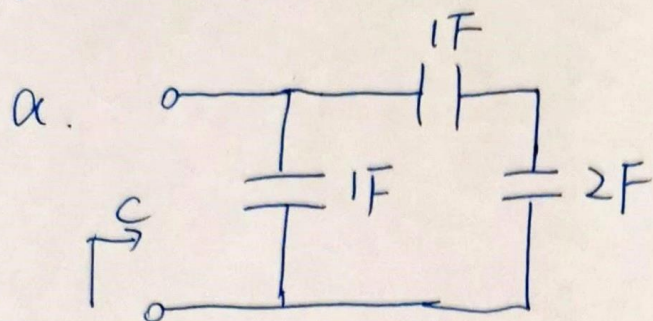
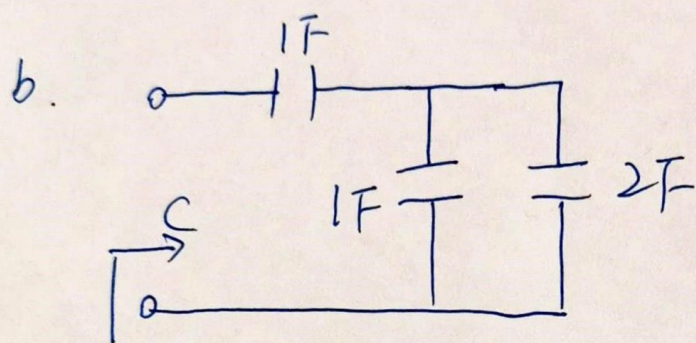
$$C = 1F + \frac{1 \times 2}{1 + 2} F = 1 + \frac{2}{3} = \frac{5}{3} F$$



$$C = \frac{1F \times 3F}{(1 + 3) F} = \frac{3}{4} F.$$