
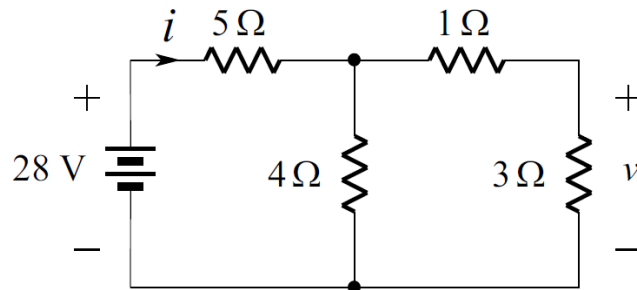


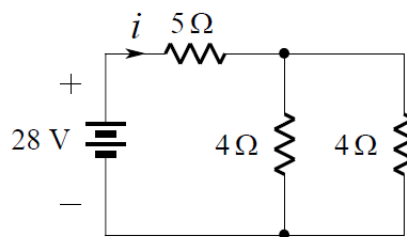
1. Please find the current i in the circuit below:



In order to find i , we can replace series and parallel connections of resistors by their equivalent resistances. We begin by noting that the 1Ω and 3Ω resistors are in series. Combining them we obtain:



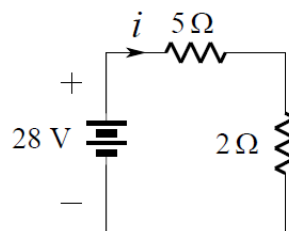
Note that it is not possible to display the original voltage v in this figure. Since the two 4Ω resistors are connected in parallel, we can further simplify the circuit as shown below:



Here, the 5Ω and 2Ω resistors are in series, so we may combine them into one 7Ω resistor. Then, from Ohm's Law, we have:

$$i = \frac{28}{7} = 4 \text{ A}$$

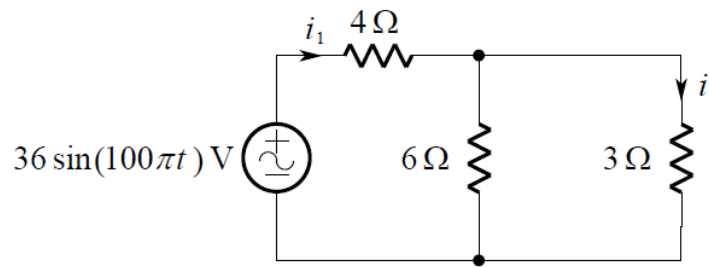2. Please find the current i in the circuit below




The total current delivered by the source is:

$$\begin{aligned} i_1 &= \frac{36 \sin(100\pi t)}{4 + (6)(3)/(6+3)} \\ &= 6 \sin(100\pi t) \text{ A} \end{aligned}$$


Therefore the desired current is:

$$i = \frac{6}{6+3} i_1 = \frac{2}{3} \times 6 \sin(100\pi t) = 4 \sin(100\pi t) \text{ A}$$

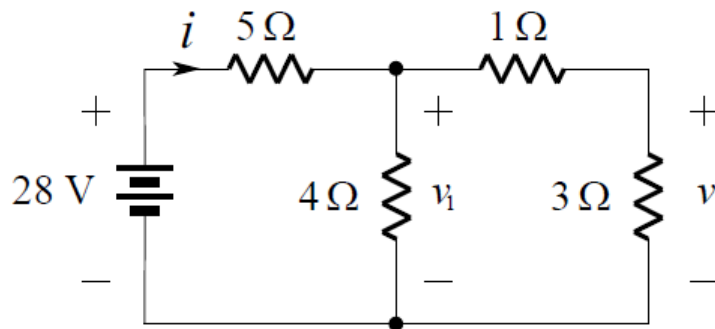
3. Please find the voltage V in the circuit below:



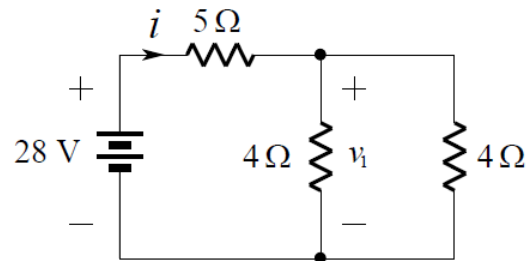Combining the series connection of the 1Ω and 3Ω resistors, we obtain the circuit below:



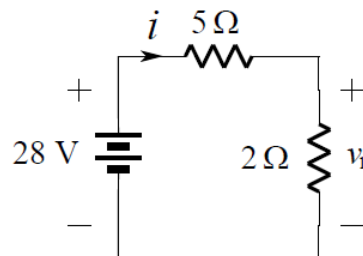Now the pair of 4Ω resistors in parallel can be combined as shown below:




By voltage division:

$$v_1 = \frac{2}{2+5} \times 28 = \frac{56}{7} = 8 \text{ V}$$

Returning to the original circuit and applying voltage division again yields:

$$v = \frac{3}{3+1} v_1 = \frac{3}{4} \times 8 = 6 \text{ V}$$

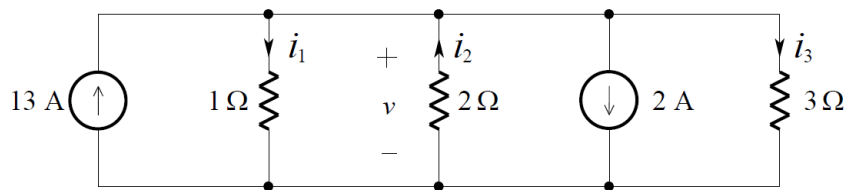4. Please find the voltage v in the two-node circuit below



The directions of i_1 , i_2 , i_3 and the polarity of v were chosen arbitrarily (the directions of the 13 A and 2 A sources are given). By KCL (at either of the two nodes), we have:

$$-13 + i_1 - i_2 + 2 + i_3 = 0$$

From this we can write:

$$i_1 - i_2 + i_3 = 11$$

By Ohm's Law:

$$i_1 = \frac{v}{1} \quad i_2 = \frac{-v}{2} \quad i_3 = \frac{v}{3}$$


Substituting these into the previous equation yields:

$$\begin{aligned} \left(\frac{v}{1}\right) - \left(\frac{-v}{2}\right) + \left(\frac{v}{3}\right) &= 11 \\ v + \frac{v}{2} + \frac{v}{3} &= 11 \\ \frac{6v + 3v + 2v}{6} &= 11 \\ \frac{11v}{6} &= 11 \\ v &= 6 \text{ V} \end{aligned}$$

Having solved for v , we can now find that:

$$i_1 = \frac{v}{1} = \frac{6}{1} = 6 \text{ A} \quad i_2 = -\frac{v}{2} = -\frac{6}{2} = -3 \text{ A} \quad i_3 = \frac{v}{3} = \frac{6}{3} = 2 \text{ A}$$

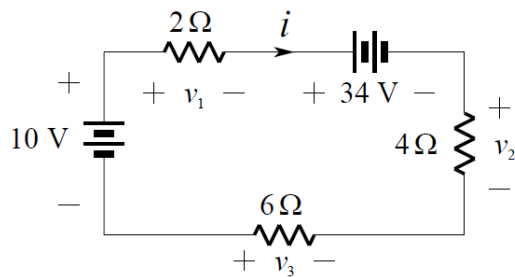5. Please find the current in the circuit below:



The polarities of v_1 , v_2 , v_3 and the direction of i were chosen arbitrarily (the polarities of the 10 V and 34 V sources are given). Applying KVL we get:

$$-10 + v_1 + 34 + v_2 - v_3 = 0$$

Thus:

$$v_1 + v_2 - v_3 = -24$$

From Ohm's Law:

$$v_1 = 2i \qquad v_2 = 4i \qquad v_3 = -6i$$

Substituting these into the previous equation yields:


$$\begin{aligned} (2i) + (4i) - (-6i) &= -24 \\ 2i + 4i + 6i &= -24 \\ 12i &= -24 \\ i &= -2 \text{ A} \end{aligned}$$

Having solved for i , we now find that:

$$\begin{aligned} v_1 &= 2i = 2(-2) = -4 \text{ V} \\ v_2 &= 4i = 4(-2) = -8 \text{ V} \\ v_3 &= -6i = (-6)(-2) = 12 \text{ V} \end{aligned}$$

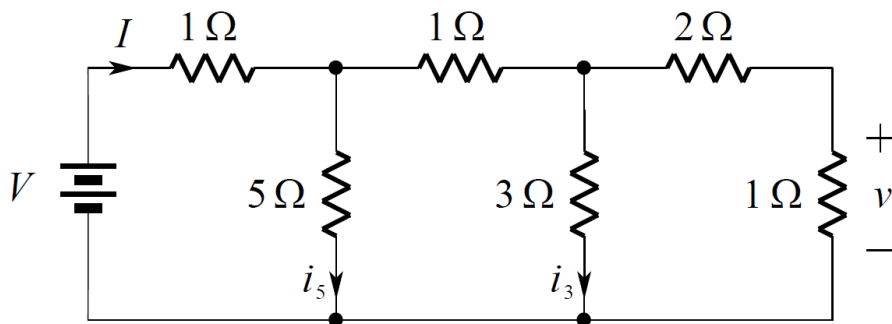6.

Given the series-parallel circuit shown below:




(a) If $v = 2$ volts, what is V ?

(b) If $i_3 = 3$ amperes, what is V ?

(c) If $i_5 = 4$ amperes, what is V ?

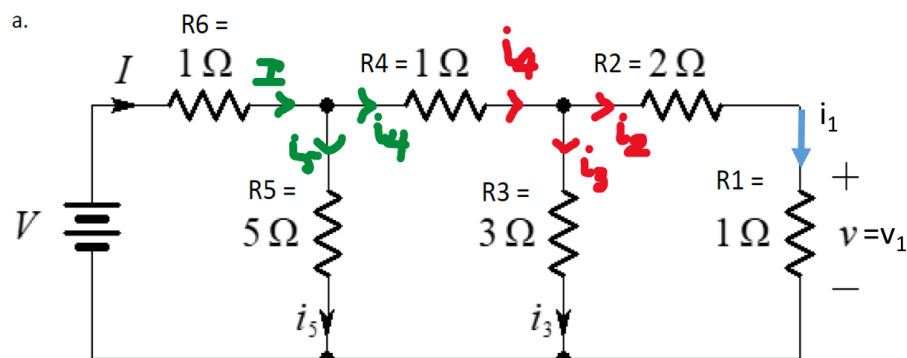(d) what is the equivalent resistance $R_{eq} = V/I$, looking from the battery?



$$v_1 = 2V \Rightarrow i_1 = \frac{v_1}{R_1} = \frac{2V}{1\Omega} = 2A$$

$$\Rightarrow i_2 = 2A \text{ (} R_1 \text{ is in series with } R_2 \text{)}$$

$$\Rightarrow v_2 = i_2 * R_2 = 2A * 2\Omega = 4V$$

$$\Rightarrow v_3 = v_2 + v_1 = 4V + 2V = 6V \text{ (} R_3 \text{ is in parallel with } R_1, R_2 \text{)}$$

$$\Rightarrow i_3 = \frac{v_3}{R_3} = \frac{6V}{3\Omega} = 2A$$

$$\Rightarrow i_4 = i_3 + i_2 = 2A + 2A = 4A \text{ (red arrows on the circuit)}$$

$$\Rightarrow v_4 = i_4 * R_4 = 4A * 1\Omega = 4V$$

$$\Rightarrow v_5 = v_4 + v_3 = 4V + 6V = 10V \text{ (} R_5 \text{ is in parallel with } R_4, R_3 \text{)}$$


$$\Rightarrow i_5 = \frac{v_5}{R_5} = \frac{10V}{5\Omega} = 2A$$

$$\Rightarrow I = i_5 + i_4 = 2A + 4A = 6A \text{ (green arrows on the circuit)}$$

$$V_6 = I * R_6 = 6V$$

$$V = v_6 + v_5 = 16V$$

b.

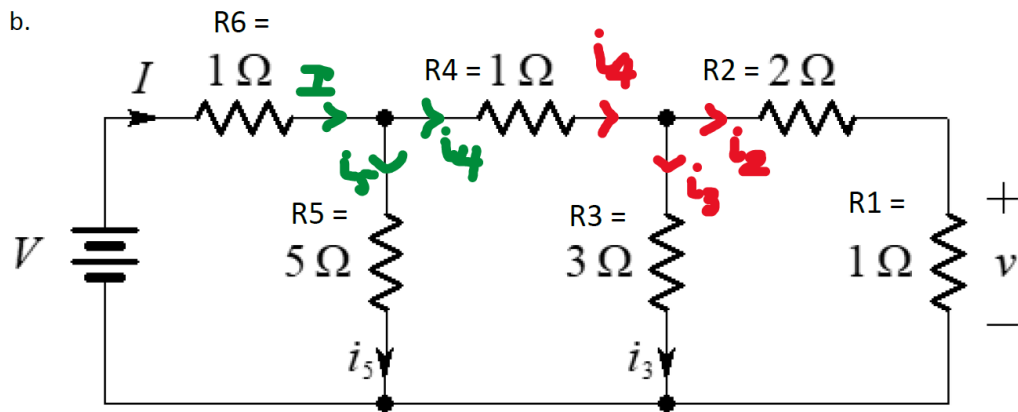

Given: $i_3 = 3A$

$$\Rightarrow v_3 = i_3 * R_3 = 3A * 3\Omega = 9V$$

$$\Rightarrow v_3 = v_{1,2} = 9V$$

$$\Rightarrow i_1 = i_2 = i_{1,2} = \frac{v_{1,2}}{R_{eq1,2}} = \frac{9V}{1\Omega + 2\Omega} = 3A$$

$$\Rightarrow i_4 = i_3 + i_1 = 3A + 3A = 6A$$

$$\Rightarrow v_4 = i_4 * R_4 = 6A * 1\Omega = 6V$$

$$\Rightarrow v_5 = v_4 + v_3 = 6V + 9V = 15V$$

$$\Rightarrow i_5 = \frac{v_5}{R_5} = \frac{15V}{5\Omega} = 3A$$

$$\Rightarrow I = i_5 + i_4 = 3A + 6A = 9A$$


$$V_6 = I * R_6 = 9V$$

$$V = v_6 + v_5 = 9V + 15V = 24V$$

c.


R1,2 is the equivalent resistance of R1 is in series with R2.
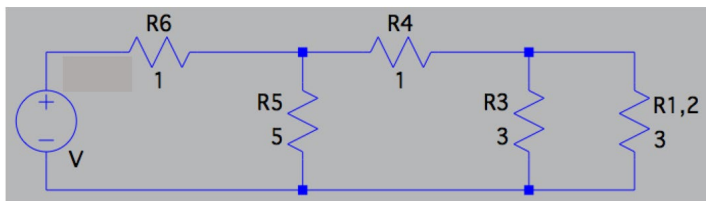
$$R_{1,2} = R_1 + R_2 = 1\Omega + 2\Omega = 3\Omega$$



R1,2,3 is the equivalent resistance of R1,2 in parallel with R3.
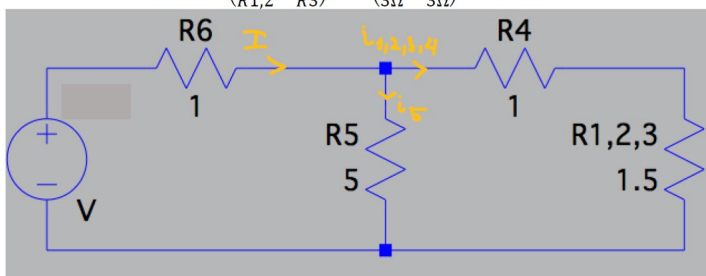
$$R_{1,2,3} = \left(\frac{1}{R_{1,2}} + \frac{1}{R_3} \right)^{-1} = \left(\frac{1}{3\Omega} + \frac{1}{3\Omega} \right)^{-1} = 1.5\Omega$$



Given: $i_5 = 4A$

$$\Rightarrow v_5 = i_5 * R_5 = 4A * 5\Omega = 20V$$

$$\Rightarrow v_5 = v_{1,2,3,4} = 20V$$

$$\Rightarrow i_{1,2,3,4} = \frac{v_{1,2,3,4}}{R_{1,2,3,4}} = \frac{20}{1\Omega + 1.5\Omega} = 8A$$

$$\Rightarrow I = i_{1,2,3,4} + i_5 = 8A + 4A = 12A$$

$$V_6 = I * R_6 = 12$$

$$V = v_6 + v_5 = 12V + 20V = 32V$$

(d)

$R_{1,2}$ is the equivalent resistance of R_1 is in series with R_2 .

$$R_{1,2} = R_1 + R_2 = 1\Omega + 2\Omega = 3\Omega$$

$R_{1,2,3}$ is the equivalent resistance of $R_{1,2}$ is in parallel with R_3 .

$$R_{1,2,3} = \left(\frac{1}{R_{1,2}} + \frac{1}{R_3} \right)^{-1} = \left(\frac{1}{3\Omega} + \frac{1}{3\Omega} \right)^{-1} = 1.5\Omega$$

$R_{1,2,3,4}$ is the equivalent resistance of $R_{1,2,3}$ is in series with R_4 .

$$R_{1,2,3,4} = R_{1,2,3} + R_4 = 1.5\Omega + 1\Omega = 2.5\Omega$$


$R_{1,2,3,4,5}$ is the equivalent resistance of $R_{1,2,3,4}$ is in parallel with R_5 .

$$R_{1,2,3,4,5} = \left(\frac{1}{R_{1,2,3,4}} + \frac{1}{R_5} \right)^{-1} = \left(\frac{1}{2.5\Omega} + \frac{1}{5\Omega} \right)^{-1} = \frac{5}{3}\Omega$$

R_{eq} is the equivalent resistance of $R_{1,2,3,4,5}$ is in series with R_6 .

$$R_{eq} = R_{1,2,3,4,5} + R_6 = \frac{5}{3}\Omega + 1\Omega = \frac{8}{3}\Omega = \frac{V}{I}$$

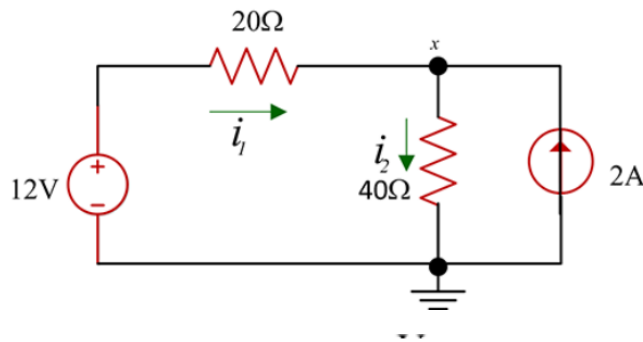7. Find the current through a 20Ω resistance, and current through a 40Ω resistance



Write KCL at node x

$$-i_1 + i_2 - 2A = 0$$

Write v_x in the circuit using Ohm's Law

$$i_1 = \frac{12V - v_x}{20\Omega}, \quad i_2 = \frac{v_x}{40\Omega}$$

Apply last two equation into KCL at node x

$$-i_1 + i_2 - 2A = -\frac{12V - v_x}{20\Omega} + \frac{v_x}{40\Omega} - 2A = 0$$

$$-0.6 + 0.05v_x + 0.025v_x - 2 = 0$$

$$v_x = 34.67V$$

The current through a 20Ω resistance


$$i_1 = \frac{12V - 34.67}{20\Omega} = -1.133A$$

The current through a 40Ω resistance

$$i_2 = \frac{v_x}{40\Omega} = \frac{34.67}{40\Omega} = 0.866A$$

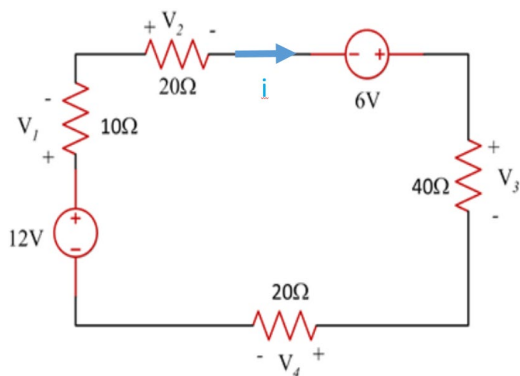8.

Find the current i and voltage v over the each resistor.



Using KVL for voltages,

$$V_1 + V_2 - 6V + V_3 + V_4 - 12V = 0$$

$$V_1 + V_2 + V_3 + V_4 = 18V$$

$$V_1 = 10 \cdot i; \quad v_2 = 20 \cdot i; \quad V_3 = 40 \cdot i; \quad V_4 = 20 \cdot i$$

Substituting into KVL equation

$$10i + 20i + 40i + 20i = 18$$

$$(90)i = 18$$


$$i = \frac{18}{90} = 0.2A$$

$$v_1 = R_1 i = 10(0.2) = 2V, \quad v_2 = R_2 i = 20(0.2) = 4V$$

$$V_3 = 8V, \quad V_4 = 4V$$

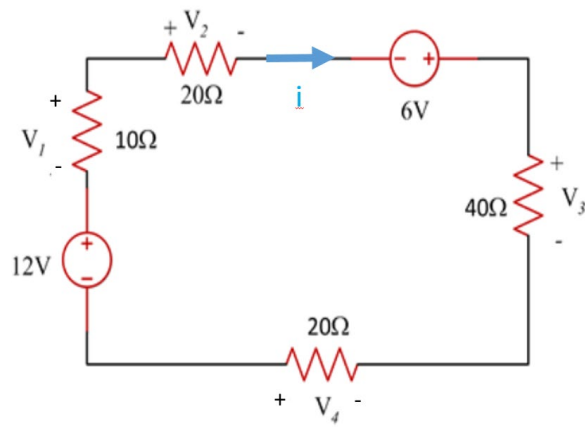9.

Find the current i and voltage v over the each resistor.



Using KVL for voltages,

$$-V_1 + V_2 - 6V + V_3 - V_4 - 12V = 0$$


$$-V_1 + V_2 + V_3 - V_4 = 18V$$

$$V_1 = 10 \cdot i; V_2 = 20 \cdot i; V_3 = 40 \cdot i; V_4 = 20 \cdot i$$

Please finish the rest by yourself

10.

Find V_0 in the following circuit.

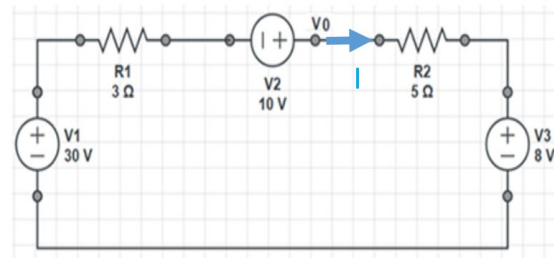


KVL Outer Loop

$$-30 - 10 + 8 + I(3 + 5) = 0$$

$$8I = 32$$

$$I = 4A$$

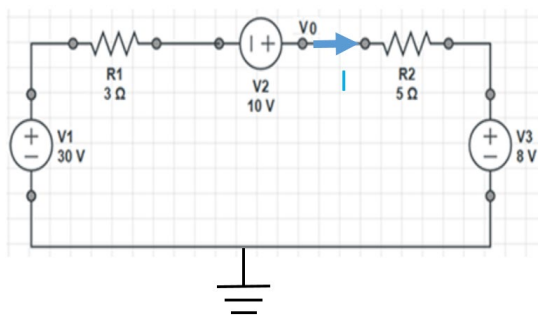Then, we assign a ground to the circuit as below:



So, $V_0 = I \cdot 5 \text{ ohm} + 8 = 28 \text{ V}$