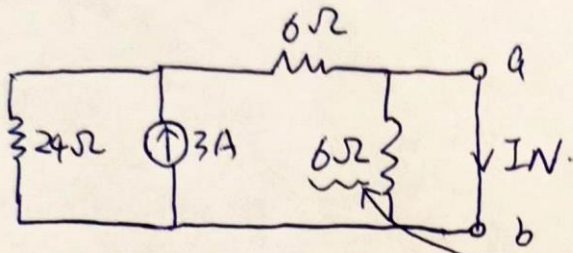



1.




a) When a b is shorted, the 6Ω is also shorted

$$\text{SO, } I_N = 3A \times \frac{24}{6+24} = 2.4A$$


By opening the current source

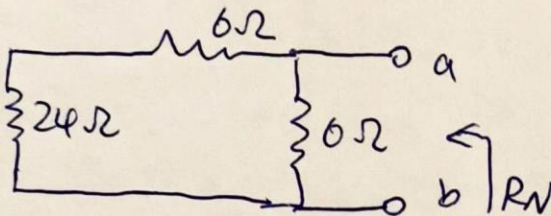

$$R_N = 6 \parallel (6+24) = 5\Omega$$

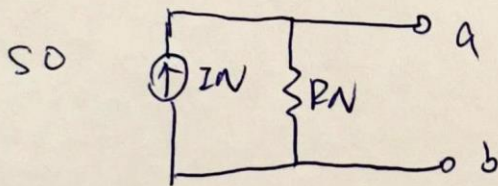

$$I_N = 2.4A \quad R_N = 5\Omega$$

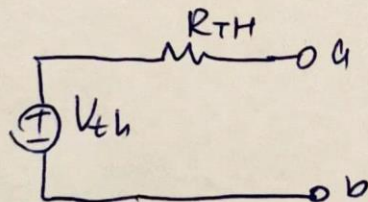

$$V_{TH} = I_N \times R_N = 5 \times 2.4 = 12V$$

$$R_{TH} = 5\Omega$$

b)



$$R_L = R_{TH} = 5\Omega$$

c) $P_{\max} = \frac{V_{th}^2}{4R_{th}} = 7.2W$

2. a) making all independent source to zero


$$R_{TH} = 1k\Omega + 2k\Omega \parallel 2k\Omega = 2k\Omega$$

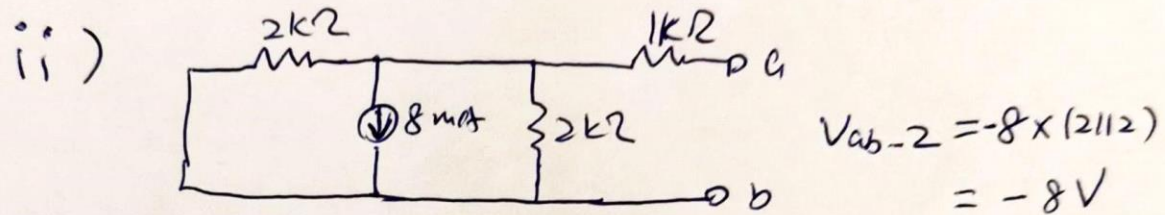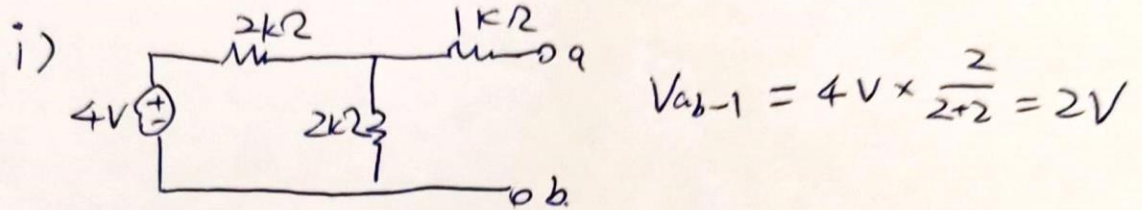b) $V_{TH} = V_{ab}$, using superposition.



SO ~~V_{ab}~~ $V_{TH} = V_{ab} = 2V - 8V = -6V$.

c) $I_N = \frac{V_{TH}}{R_{TH}} = -3mA$

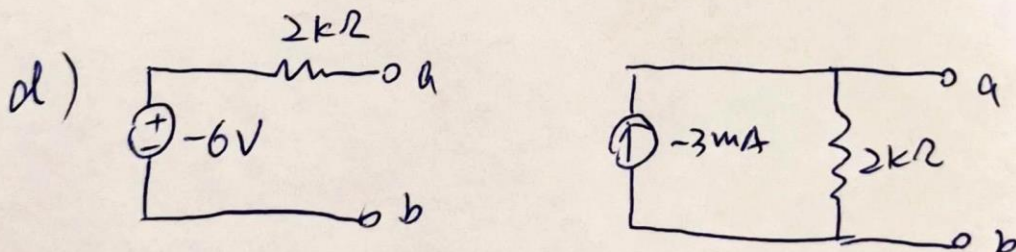

e)

$$I_{load} = \frac{2}{2+4} \times (-3mA) = -1mA$$

f) $R_L = R_{TH} = 2k\Omega$

g) $P_{max} = \frac{V_{th}^2}{4R_{th}} = 9/2 \text{ mW}$