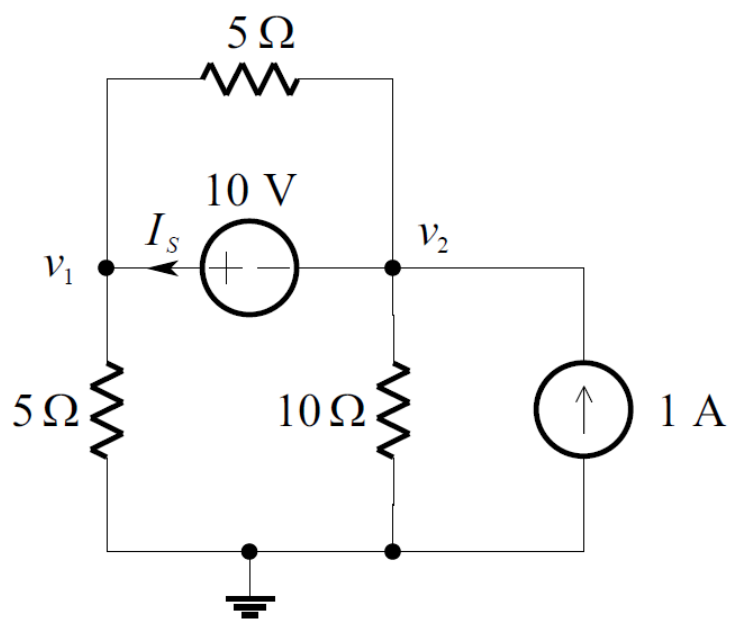


Nodal and Mesh Analysis

1.

Find the nodal voltages in the circuit below, and hence the value of I_s .



2.

Find the current in each resistor in the circuit below.

