

Capacitors

1.

Suppose that the voltage $v(t)$ shown below is applied to a $200\text{ }\mu\text{F}$ capacitor.

- a) Plot the current through the capacitor versus time.
- b) Plot the power delivered to the capacitor versus time.
- c) Find the stored energy at $t = 3\text{ s}$.

