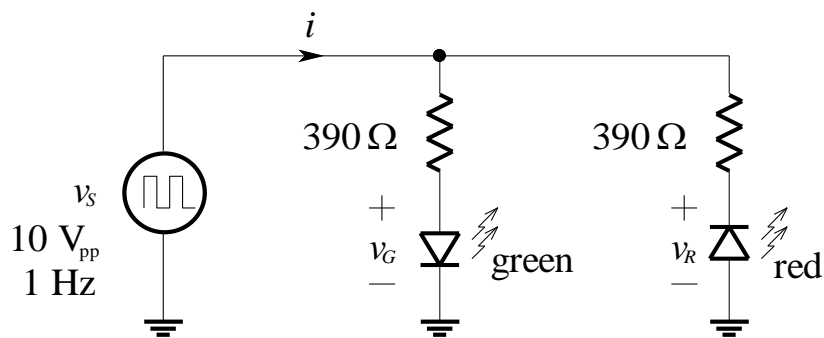


# Diode Circuits

1.


The circuit below uses LEDs which can be modelled using the “constant voltage drop model” with  $e_{fd} = 2.0\text{ V}$ . The source voltage is a square wave with a  $10\text{ V}$  peak-to-peak amplitude, centred around  $0\text{ V}$ .



- (a) Sketch the voltage waveforms (vs. time) for  $v_G$  and  $v_R$ .
- (b) If you built the circuit, what would you see?

2.

Consider the circuit shown below:

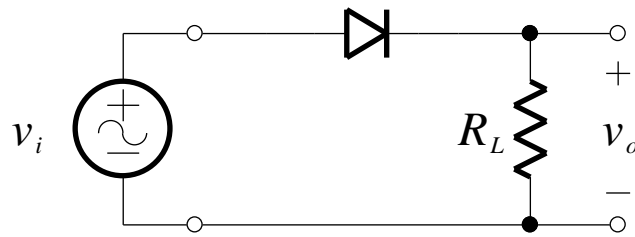

Assume that the diode can be modelled using the “constant voltage drop model” with  $e_{fd} = 0.7 \text{ V}$ .

Given that  $v_i(t) = 5 \sin(500\pi) \text{ V}$  and load resistance  $R_L = 1 \text{ k}\Omega$ :

- (a) Plot  $v_i(t)$  and  $v_o(t)$  on the same graph.
- (b) What is the peak load current?