

## Week-1 Tutorial

1.


The current through a given circuit element is given by  $i(t) = 2e^{-t}$  A. Graph the current and find the net charge that passes through the element in the interval from  $t = 0$  to  $t = \infty$ .

2.

Compute the resistance of a copper wire having a diameter of 1.5 mm and a length of 5 m, given  $\rho_{\text{copper}} = 1.7 \times 10^{-8} \Omega \cdot \text{m}$ .

3.

Consider the circuit shown below:

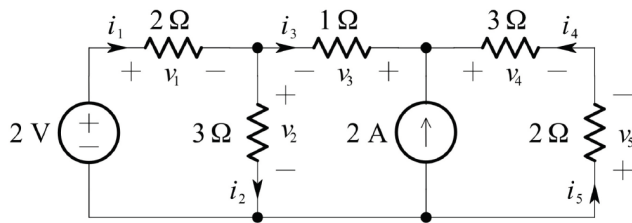

(a) If  $v_1 = -\frac{2}{3}$  V, find  $i_1$ .

(b) If  $v_2 = \frac{8}{3}$  V, find  $i_2$ .


(c) If  $v_3 = \frac{11}{9}$  V, find  $i_3$ .

(d) If  $v_4 = \frac{4}{3}$  V, find  $i_4$ .

(e) If  $v_5 = -\frac{14}{9}$  V, find  $i_5$ .

4.

Consider the circuit shown below:

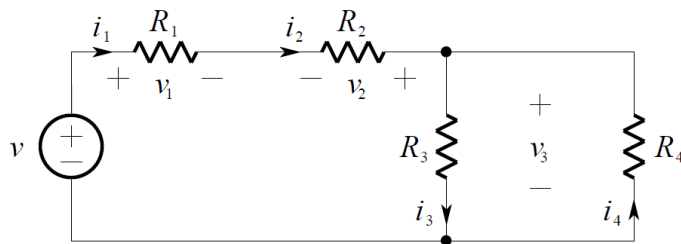

(a) If  $i_1(t) = -e^{-2t}$  and  $v_1(t) = -2e^{-2t}$ , find  $R_1$ .

(b) If  $i_2(t) = -e^{-2t}$  and  $v_2(t) = 6e^{-2t}$ , find  $R_2$ .

(c) If  $i_3(t) = -\frac{2}{3}e^{-2t}$  and  $v_3(t) = -2e^{-2t}$ , find  $R_3$ .

(d) If  $i_4(t) = \frac{1}{3}e^{-2t}$  and  $v_3(t) = -2e^{-2t}$ , find  $R_4$ .

5. The total charge  $q(t)$  in some material is described by the function given below:

Find the current  $i(t)$  and draw it.

